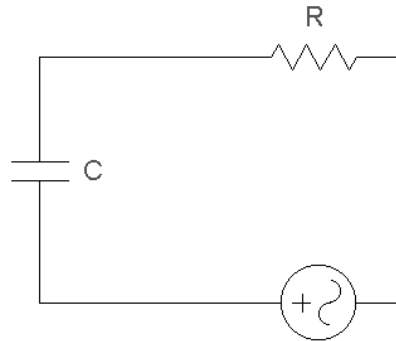


# BAGIAN 4

## PRINSIP DASAR FILTER AKTIF MENGUNAKAN OP-AMP

### Karakteristik Kapasitor



Reaktansi Kapasitif :  $X_C = 1/2\pi fC = 1/\omega C$


Impedansi :  $Z = \sqrt{R^2 + X_C^2}$

Phase :  $\theta = \cos^{-1} (R/Z)$

### Representasi Spektrum Frekuensi




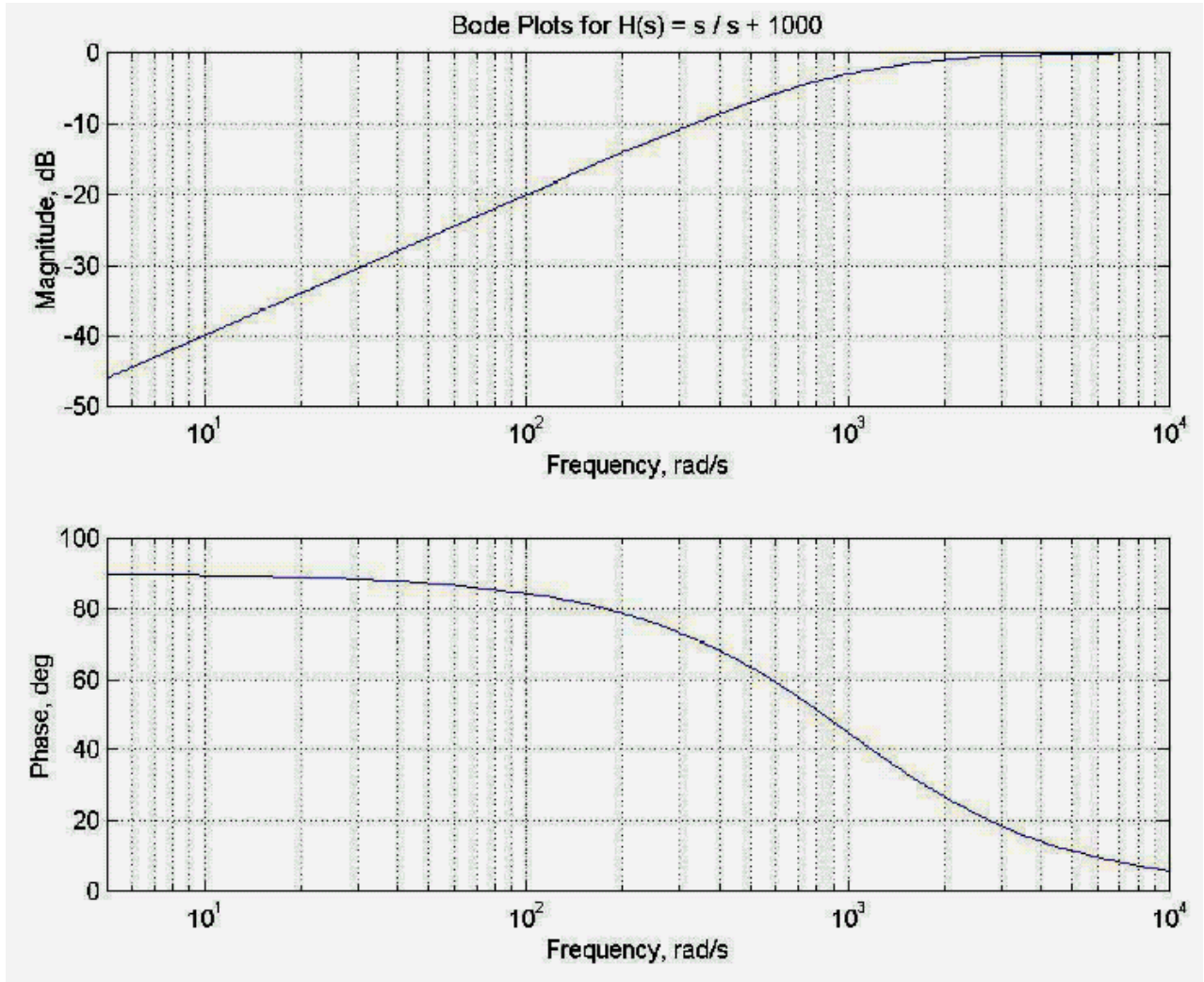**Representasi Spektrum Frekuensi (Diagram Bode)**




Magnitude = Penguatan (dalam satuan dB) =  $20 \log H(j\omega)$

$$H(j\omega) = Y(j\omega) / X(j\omega)$$

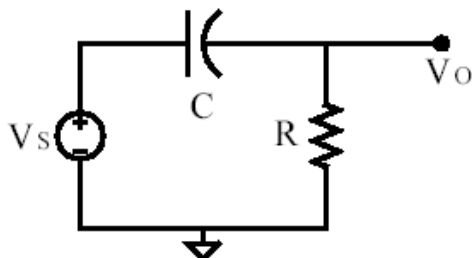


High Pass Filter

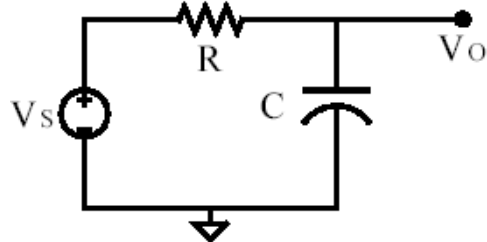


Low Pass Filter

Cutoff Frequency :  $\omega_c = 1/RC$

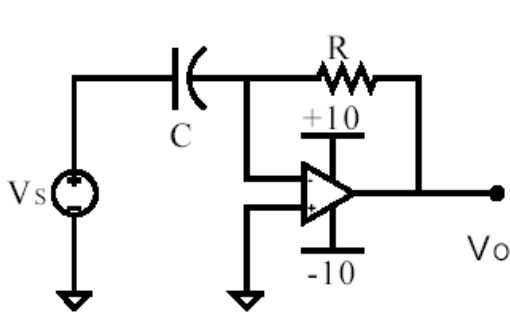

Diferensiator

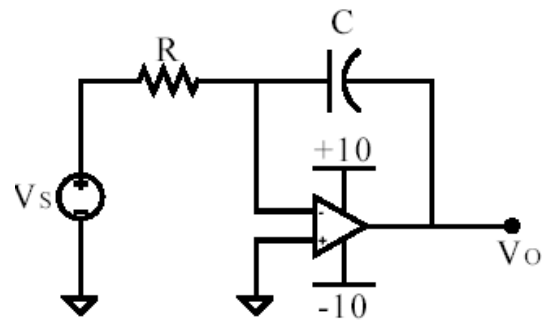

Integrator

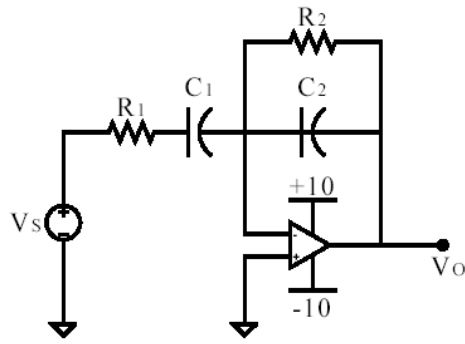


Figure 9. An Active Band Pass Filter.

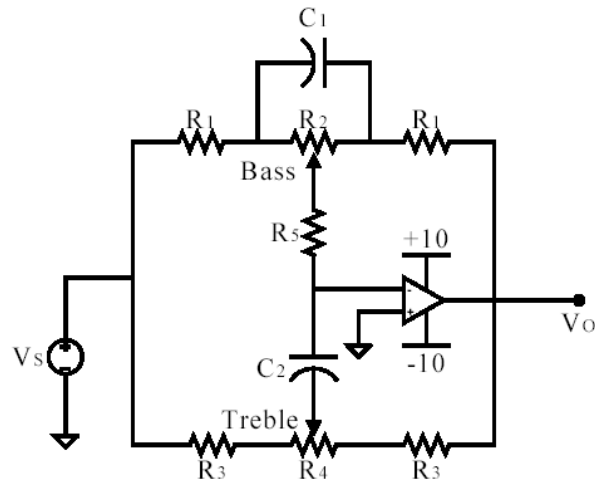


Figure 10. Bass and Treble Control.

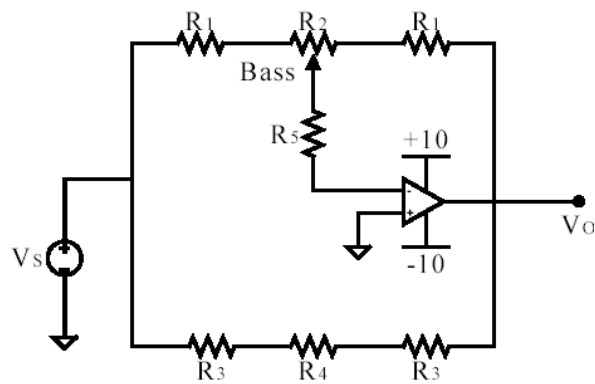


Figure 11. Bass Controller at Low Frequencies.

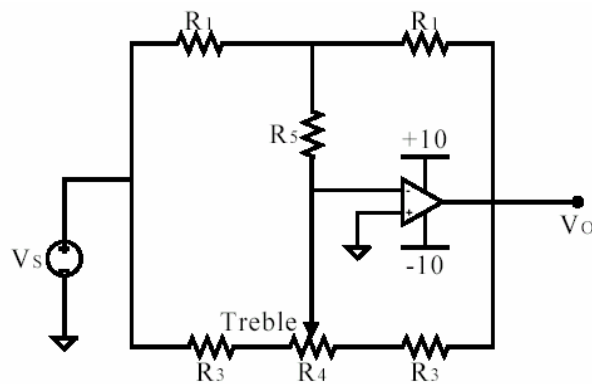


Figure 12. Treble Controller at High Frequencies.